

TMC262-LA STEPPER MOTOR PRE-DRIVER

Product Training Module (PTM)



TMC262 – GETTING STARTED

The TMC262 is a pre-driver for two-phase stepper motors.

The TMC262 offers an industry-leading feature set, including high-resolution micro-stepping, sensorless mechanical load measurement, load-adaptive power optimization, and low-resonance chopper operation. Standard SPI™ and STEP/DIR interfaces simplify communication.

The TMC262 drives four external N- and P-channel dual MOSFETs for motor currents up to 8A and up to 60V. Integrated protection and diagnostic features support robust and reliable operation.

Typical applications:

Textile, Sewing Machines / Factory Automation / Lab Automation / Liquid Handling / Medical / Office Automation / Printer and Scanner / CCTV, Security / ATM, Cash recycler / POS / Pumps and Valves / Heliostat Controller / CNC Machines

GENERAL SYSTEM ARCHITECTURE



WHAT IS REQUIRED FOR A STANDARD SETUP?



HOW TO SELECT R_{SENSE}?

$$R_{sense} = \frac{248}{256} * \frac{(CS+1)}{32} * \frac{V_{FS}}{I_{rms}} * \frac{1}{\sqrt{2}}$$

$$P_{RSMAX} = \frac{\left(V_{FS} * \frac{CS + 1}{32}\right)^2}{R_{SENSE}}$$

Use CS = 31 and VSENSE = 0 ($V_{FS} = 310mV$), and your required absolute maximum RMS current for calculation.

Example: $I_{RMS} = 2.1A$ $\rightarrow R_{sense} = 99.5m\Omega \approx 100m\Omega$ $\rightarrow P_{RSMAX} = 0.961W$

HOW TO SELECT MOSFETS?

- 1. Select an appropriate Motor voltage range
- 2. Gate Charge $Q_{GD} < 20nC$ at 5V
- 3. Threshhold Voltage $1V < V_{TH} \ll 5V$
- 4. Select $R_{DS_{ON}}$ according to the required gate current and acceptable powr dissipation at the power stage.
- 5. Check if the nominal current rating of the MOSFET manufacturer matches your requirements

Use the TMC262 spreadsheet to calculate power dissipation of the TMC262 driver *stage* with your application and MOSFET parameters: <u>download link</u>

INTERNAL OR EXTERNAL CLOCK?

- Internal CLK is ca.15 MHz / external CLK range: 4MHz to 20 MHz
- Why using internal CLK ?
 - Standalone operation, save extra CLK source, good choice for most applications
- Why using external CLK ?
 - For well defined precise motor chopper operation, an external clock source with stable and known frequency is suggested
 - Higher CLK frequency allows for faster step rates, faster SPI operation, and higher chopper frequencies but may also cause more electromagnetic emission and more power dissipation.
 - Use same CLK base as other ICs in the application
 - Can be derived from a microcontroller, does not require extra part
- If the application can tolerate reduced motor velocity and increased chopper noise, a clock frequency of 4MHz to 10MHz should be considered.
- Generally, a system clock frequency of 10MHz to 16MHz should be sufficient for most applications.
- A chopper frequency > 16MHz is suggested when operating a motor at the highest velocities.

TMC262 - BOM EXAMPLE

Typical Setup for 48V supply voltage and 2.1A (RMS) Phase-Current

PCS	POS	Name/ Type	Value	Digi-Key Part #
1	IC1	TMC262-LA		1460-1044-ND
2	R1,R2	SMD Sense Resistor	100 mΩ, 1W, 1%	311-0.1ARTR-ND
4	T1, T1, T3, T4	AO4612	MOSFET N/P	785-1041-2-ND
1	C1	Ceramic Capacitor	220nF/16V	399-5619-2-ND
1	C2	Ceramic Capacitor	100nF	399-7371-2-ND
1	C3	Ceramic Capacitor	470nF	399-4922-1-ND
2	C4, C5	Ceramic Capacitor	100nF/63V	311-1523-2-ND
1	C6	Electrolyte Capacitor	220µF/63V	P5194-ND

Placement:

- Sense resistors should be placed close to the MOSFETs and close to the driver IC (green)
- Place filter capacitors as close as possible near the driver's interface pins (blue).
- Focus on a symmetric placement and layout for sense resistors and MOSFETs



Ground connections

- For optimum cooling and ground connection a 4 Layer Design is recommended
- use one layer as solid GND plane
- Package bottom pad connected to all GND pins
- Use a couple of vias to GND layer for bottom pad
- Use the bottom layer for cooling areas for the MOSFETs and signal routing



Top layer (assembly side)



Bottom layer

Sense Resistor Connection

- Use vias at sense resistor terminals to GND layer
- Use wide / short traces with only less bends to the full bridge foot points
- The two sense resistors should NOT share a common ground connection trace.
- No current other than the sense resistor currents should flow through their connections to ground



Top layer (assembly side)



 $V_{\rm m}$ layer



top layer (assembly side)

bottom layer (solder side)

TMC262 – INITIAL CONFIGURATION

Chopper control register (CHOPCONF):

SPI = \$901B4 // Use hysteresis mode chopper

stallGuard2 and current control register (SGCSCONF):

SPI = \$D001F // Current setting: \$d001F (maximum current)

Driver control register (DRVCONF):

SPI = \$EF010 // high gate driver strength, stallGuard read, SDOFF=0

Driver control register (DRVCTRL):

SPI = \$00000 // 256 microstep setting

coolStep control register (SMARTEN):

SPI = \$A8202 // enable coolStep with minimum current = 1/4 of max. I